 


# **Design and Implementation of an RTL FIFO Queue with Push/Pop Operations, Error Detection**

**KARNATI AMULYA  
NAUREEN NAAZ  
PULAK MISHRA  
PURVI P**




# Project Objective and FIFO Overview


 
## Objectives :

To design a synchronous FIFO queue with:

- Push/Pop operations
- Overflow/Underflow error detection
- Status flag management (full, empty)



## FIFO (First-In First-Out):

- A type of queue where data exits in the order it was entered.
- Widely used in buffering, streaming, and inter-module communication



01

### Modules Used:

- fifo\_mem: memory array
- write\_ptr, read\_ptr: pointers for tracking position
- fifo\_count: keeps track of number of stored items

03

### Status Flags:

- full: high when FIFO is full
- empty: high when FIFO is empty

02

### Control Signals:


- push for writing
- pop for reading


04

### Error Flags:

- overflow\_error: raised if push attempted when full
- underflow\_error: raised if pop attempted when empty

# RTL FIFO Design

 

 

# VERILOG CODE HIGHLIGHTS :



## MEMORY DECLARATION

```
reg [7:0] fifo_mem [0:FIFO_DEPTH-1];
```

## PUSH LOGIC


```
always @(posedge clk or posedge rst) begin
    if (rst) begin
        write_ptr <= 0;
        overflow_error <= 0;
    end else if (push) begin
        if (full) begin
            overflow_error <= 1;
        end else begin
            fifo_mem[write_ptr] <= data_in;
            write_ptr <= write_ptr + 1;
            overflow_error <= 0;
        end
    end
end
```

## POP LOGIC

```
always @(posedge clk or posedge rst) begin
    if (rst) begin
        read_ptr <= 0;
        underflow_error <= 0;
        data_out <= 0;
    end else if (pop) begin
        if (empty) begin
            underflow_error <= 1;
        end else begin
            data_out <= fifo_mem[read_ptr];
            read_ptr <= read_ptr + 1;
            underflow_error <= 0;
        end
    end
end
```
 
## STATUS FLAG LOGIC

```
full  = (fifo_count == FIFO_DEPTH);
empty = (fifo_count == 0);
```



# TESTBENCH



## Clock and Reset Generation

```
initial clk = 0;  
always #5 clk = ~clk;
```

- Clock is generated with a period of 10 ns.
- Reset initializes all the FIFO registers and pointers.

## Push Task


```
task do_push(input [7:0] value);  
begin  
    @(posedge clk);  
    push <= 1;  
    data_in <= value;  
    @(posedge clk);  
    push <= 0;  
end  
endtask
```

- Simplifies the testbench by allowing you to call do\_push(value) to insert a byte into the FIFO.
- Push operation is synchronized to the clock edges.

 
## Pop Task



```
task do_pop;  
begin  
    @(posedge clk);  
    pop <= 1;  
    @(posedge clk);  
    pop <= 0;  
end  
endtask
```

- Reads data from the FIFO one clock cycle at a time.



# SIMULATION :

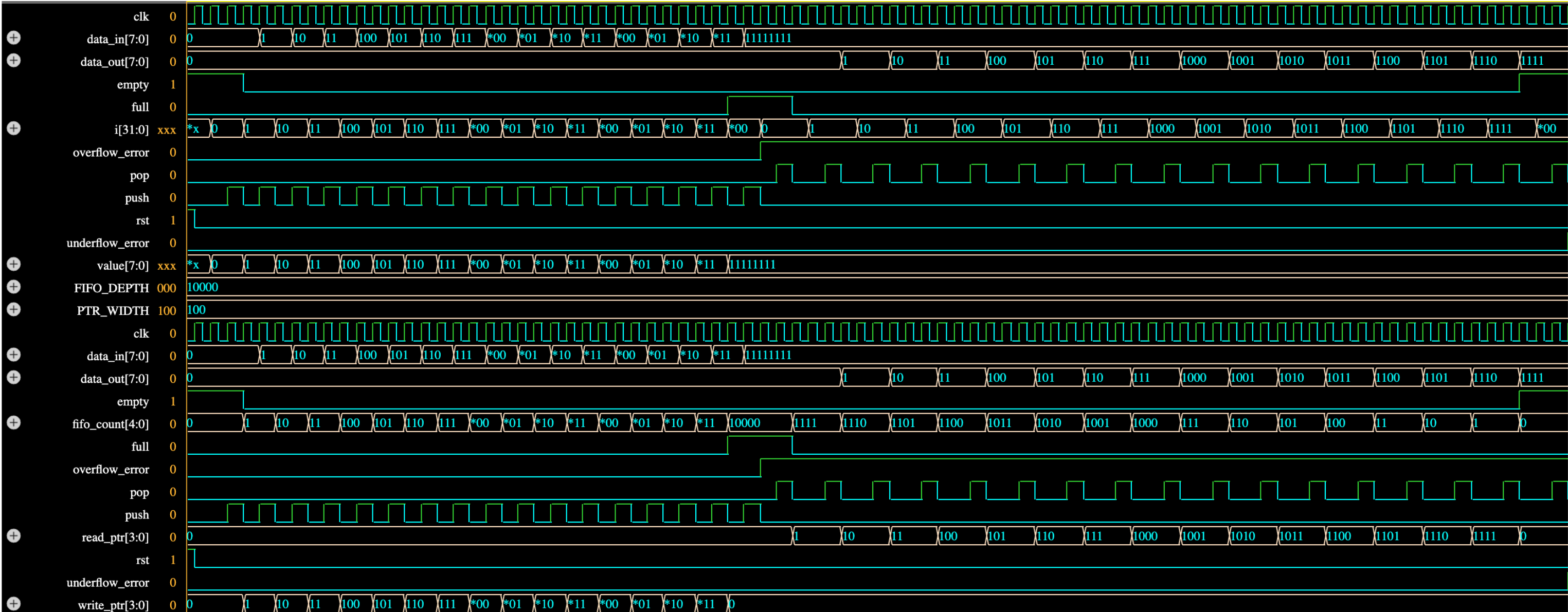

  

# APPLICATIONS

1. Data Buffers in Communication Systems
2. DMA (Direct Memory Access) Controllers
3. Processor Pipelining
4. Real-Time Data Logging
5. Audio/Video Streaming
6. Asynchronous Clock Domain Crossing (CDC)

